

Name:




Date:

TA:

Learning Guide 9

Power, Energy, and Complex Circuits Notes

We have learned about Voltage, Current, and Resistance so far. However, electricity is a type of energy, and we have yet to see a way to measure energy or how fast we use it. Therefore, we will look at two more equations, each with a new math triangle.

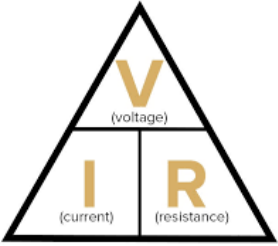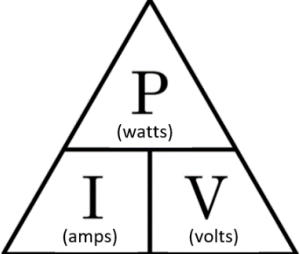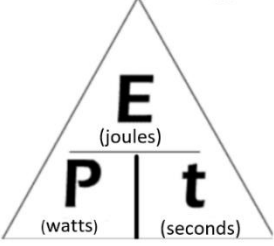		
<p>$I = V \div R$ Where:</p> <ul style="list-style-type: none"> I is current, the speed of electrons (Amps or milliamps) V is voltage (potential difference), the pushing power (Volts) R is resistance, the force against the flow of electrons (Ohms) 	<p>$I = P \div V$ Where:</p> <ul style="list-style-type: none"> I is current, the speed of electrons (Amps or milliamps) V is voltage (potential difference), the pushing power (Volts) P is power, the speed/rate that energy is being used/transferred (Watts) 	<p>$P = E \div t$ Where:</p> <ul style="list-style-type: none"> P is power, the speed that energy is being used/transferred (Watts) t is time, the amount of time a circuit runs or electricity is transferred (seconds) E is energy, the amount of energy that has or is being used based on quick it is being used and the time (Joules)

These three triangles can help use determine how much energy is being used. For example:

- 1) If a circuit has 5 Ω of **resistance** and 3 A of **current**, how much energy is used when the circuit is live for 5 **seconds**?

Let's use the first triangle to find the voltage:

Now that we have voltage, let's use the second triangle to find power:

Name:

Date:

TA:

Now that we have power, let's use the third triangle to find energy:

Please note: a **Joule** is really small, as it is **Watts times Seconds**. Electric companies charge in **Kilowatts times Hours**, as that unit is much bigger can be used to describe large usage of energy, such as the amount of energy used in a home over 2 months.

- 2) A circuit runs using 110 V and 500 mA of current. When used for 2 minute, what is the total amount of energy used?

We need to start by converting mA to A:

Then, find the power:

Then, find the energy used in 2 minutes. 1 minute has 60 seconds.

- 3) If a circuit has 2000 mA of current and uses 800 J of energy in 10 seconds, what is the total resistance in the circuit?

Name:

Date:


TA:

Extending: Complex circuits are circuits that have both parallel and series components to them. If 1 resistor leads to another on the same path, the resistors are in parallel. If 1 resistor is on a separate path compared to another resistor, they are in parallel.


Your parallel circuit rules apply to resistors/batteries in parallel, and your series circuit rules apply to resistors/batteries in series.

Sometimes it helps to redraw a circuit diagram in a way that pretends two resistors are acting like a single resistor. That way, you can more easily visualize that resistors are acting in series or parallel.

Example 1:

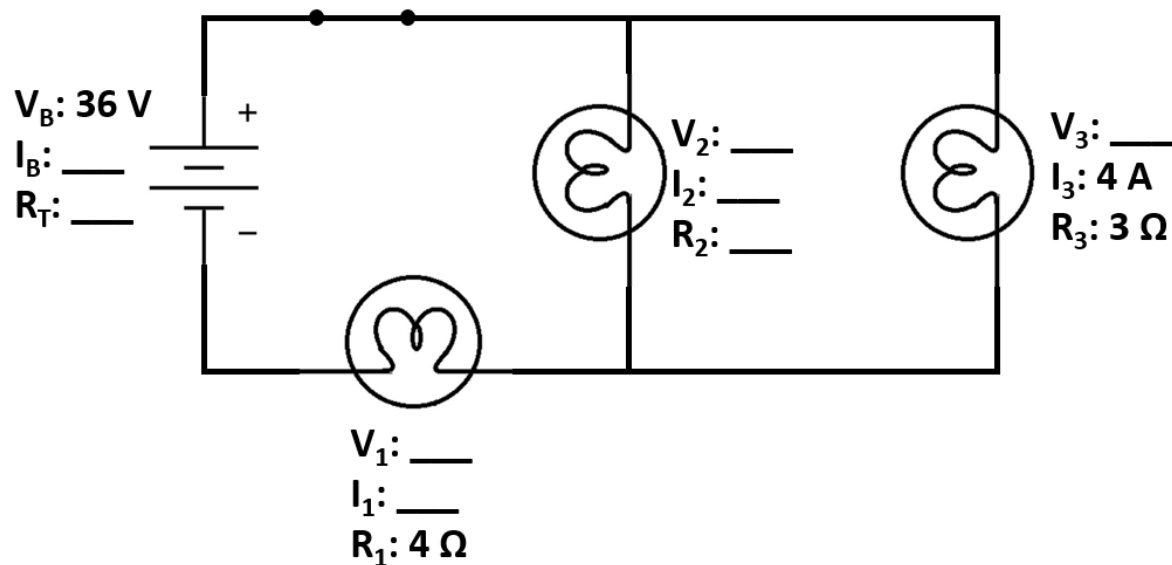

Example 2:

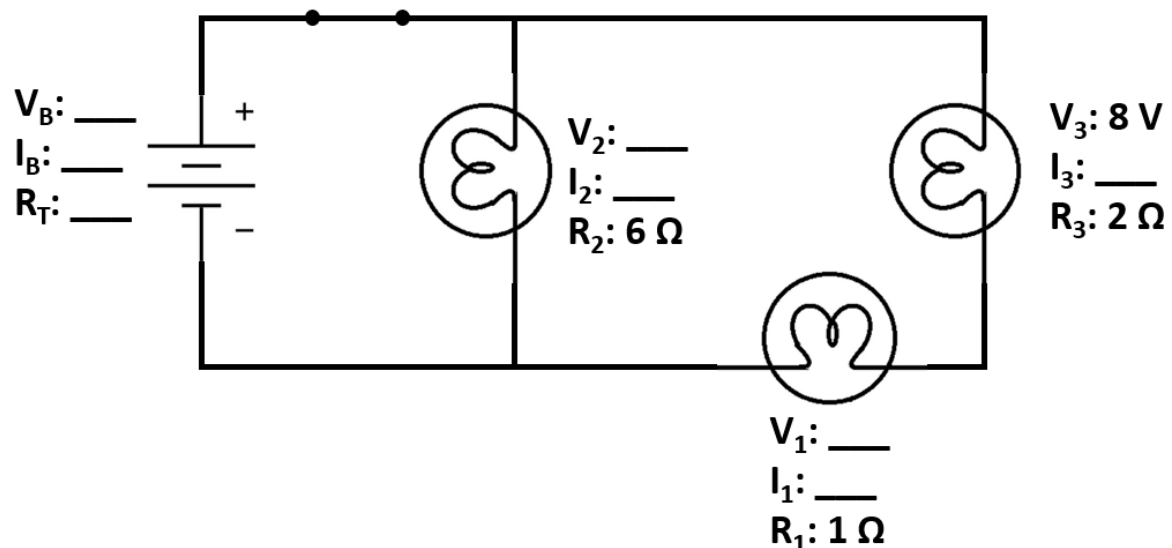


Name:

Date:

TA:

Example 3:

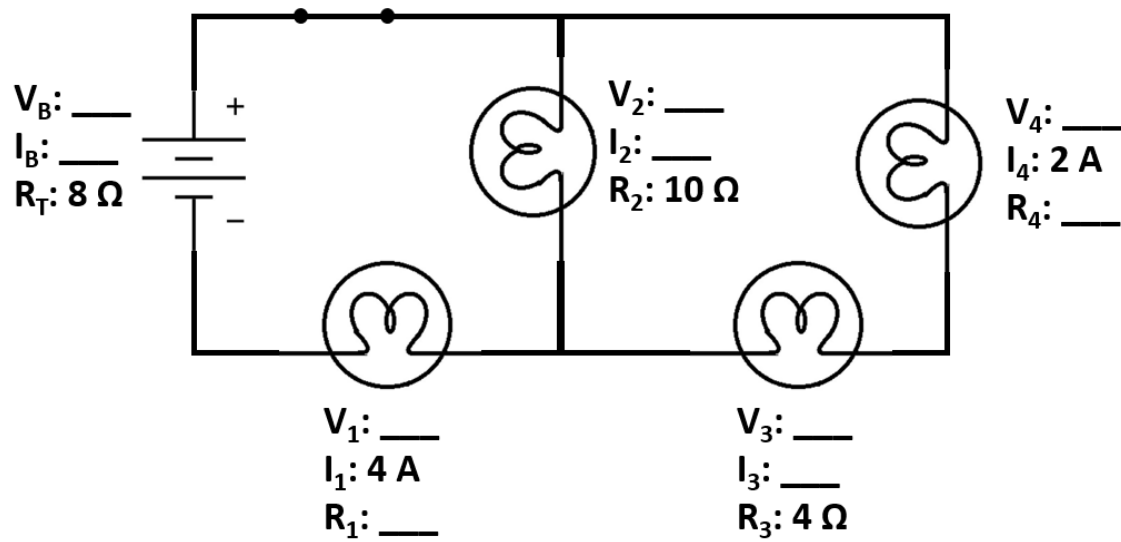

Example 4:

